

Circuit Diagram

Read the specifications and draw circuits.

- 1) Draw a circuit that has a cell, an open switch, and one light bulb connected in a series.

2) D
se

Preview

3) D
th

**Become a member to unlock
unrestricted access to both printable
and online worksheets.**

b on

www.tutoringhour.com



- 4) Draw a circuit that has a cell, a closed switch, and two bulbs connected in a series.