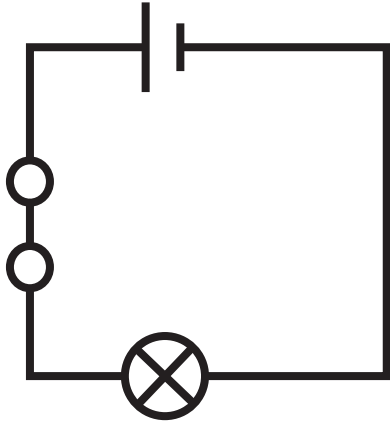



# Open and Closed Circuits

Observe each diagram and label the circuit as open or closed.


1)




2)

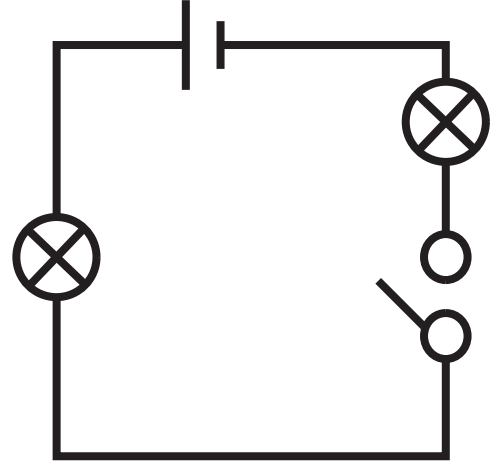


3)

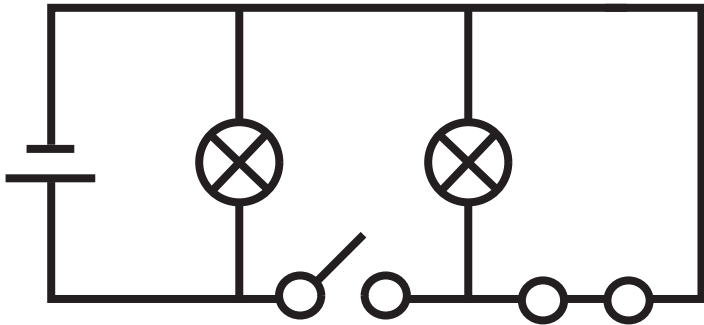

4)

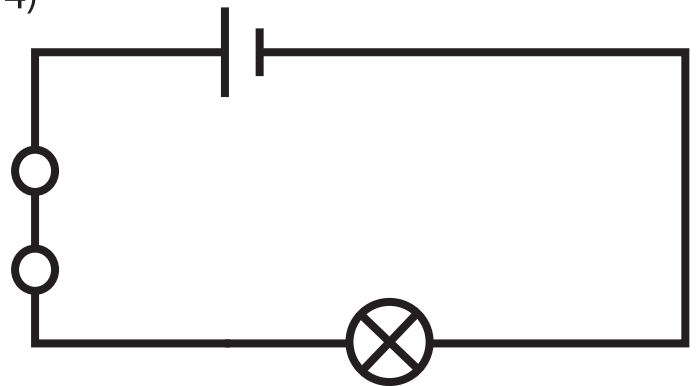

5)

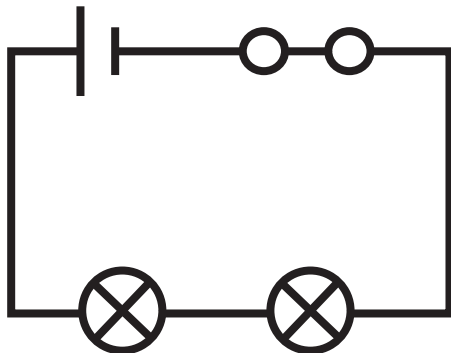

6)

