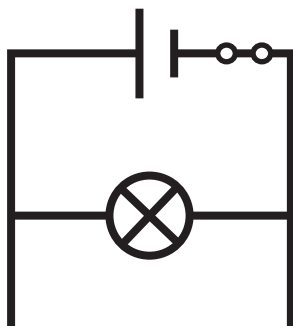



Series and Parallel Circuits

Observe each circuit and label it as series or parallel.


1)



2)

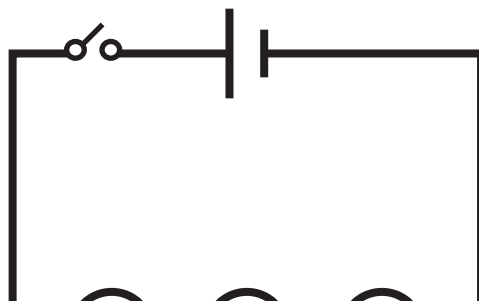

3)

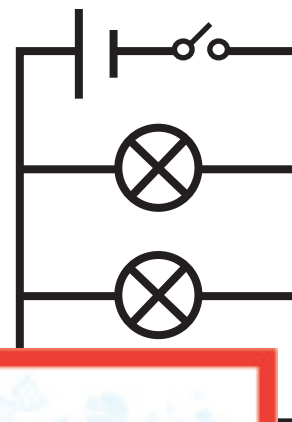


4)

**Become a member to unlock
unrestricted access to both printable
and online worksheets.**




www.tutoringhour.com

7)

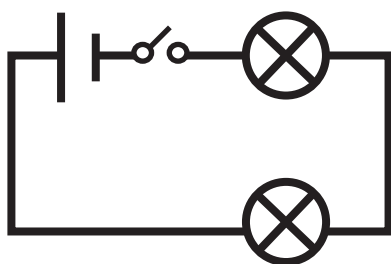

8)

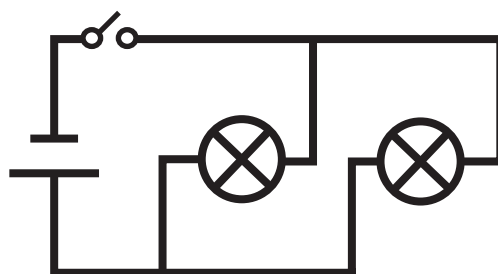

9)

