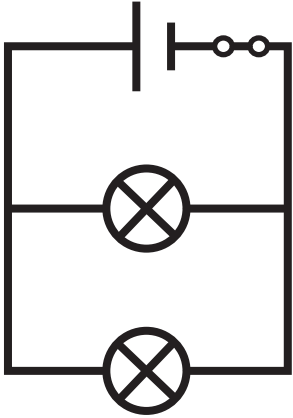



Series and Parallel Circuits

Observe each circuit and label it as series or parallel.


1)




2)

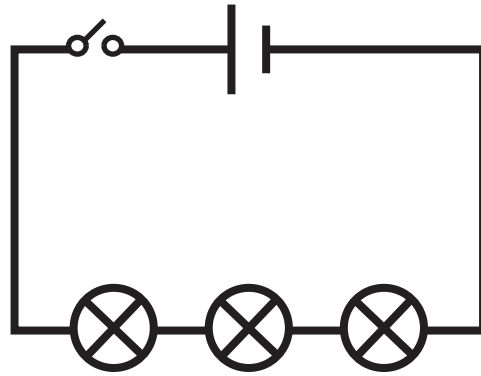


3)

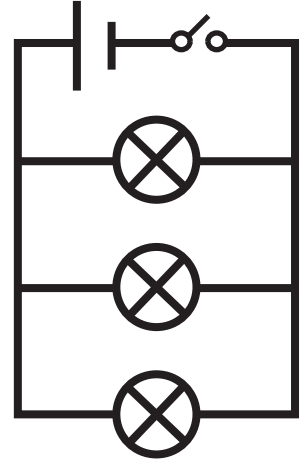


4)

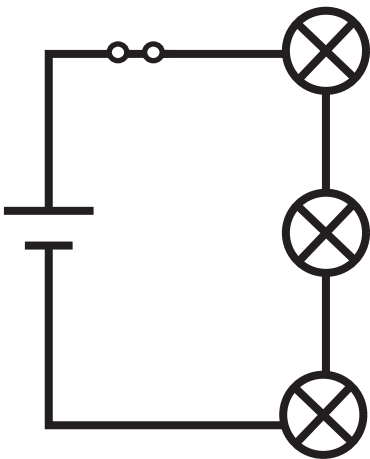


5)

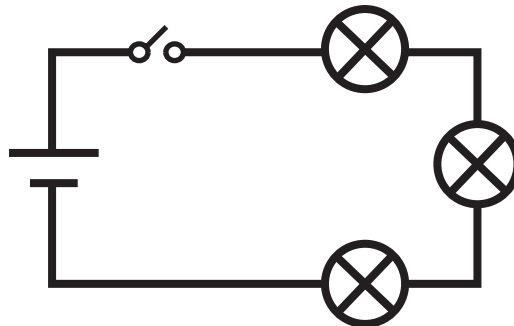


6)

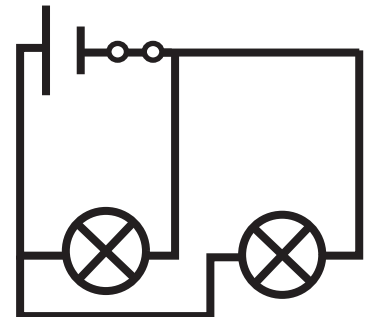

7)

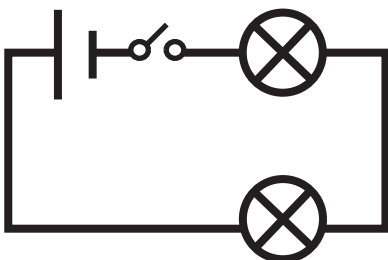

8)

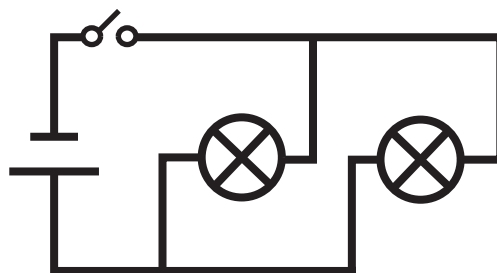

9)

